
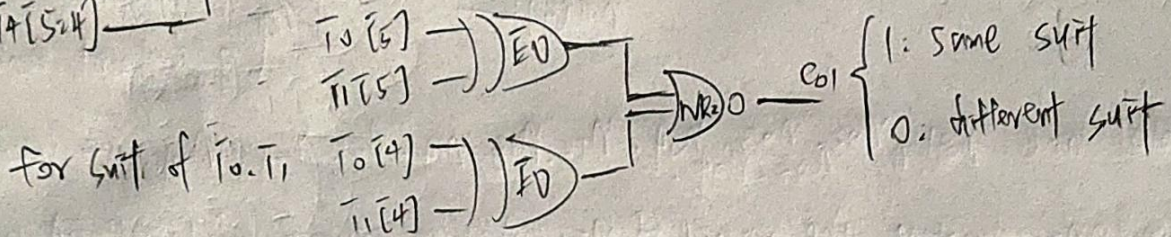



module : Flush

result = 1 \Rightarrow suit is the same

result = 0 \Rightarrow suit is different

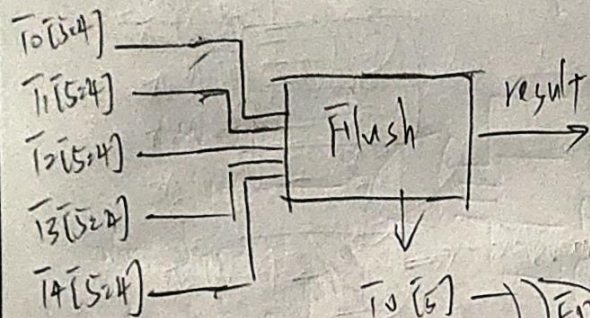



module : rank type

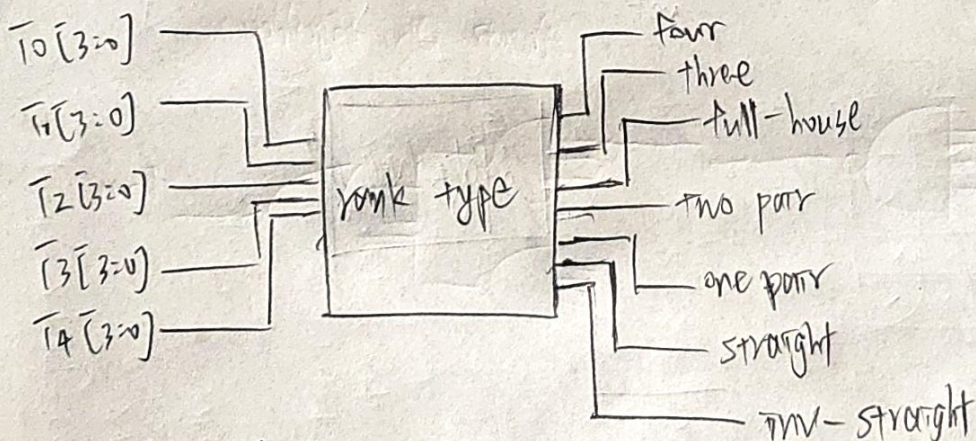

if four / three / full-house / two pair / one pair / straight = 1
 \Rightarrow denoting the corresponding type

inv-straight = (straight)'

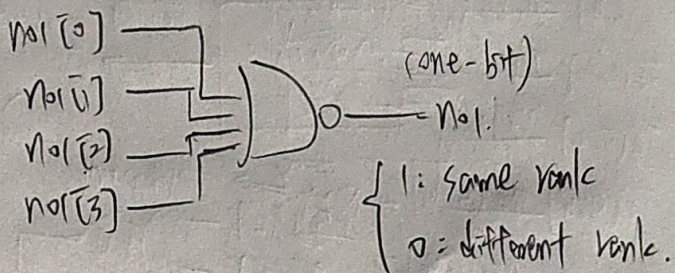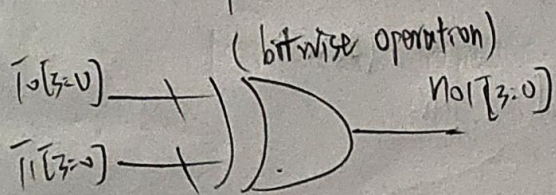first need to check $C_2^5 = 10$ pairs. if the rank of each pair is same
 for example: check if $T_0[3:0]$. $T_1[3:0]$ have the same rank.



→ total have $No1, No2, No3, No4, N_{12}, N_{13}, N_{14}, N_{23}, N_{24}, N_{34} = 10$ result

→ $inv - n_{ij}$ denoting the inverse of n_{ij} . that is $inv - No1$ { 1: different rank
 0: same rank.
 ($n_{ij} \rightarrow 0 \rightarrow inv - n_{ij}$)


* for output "four" → check $C_4^5 = 5$ cases

that is: 0123/4, 0124/3, 0134/2, 0234/1, 1234/0

for example: 0123/4:


after get all result of 5 cases

→ OR together:

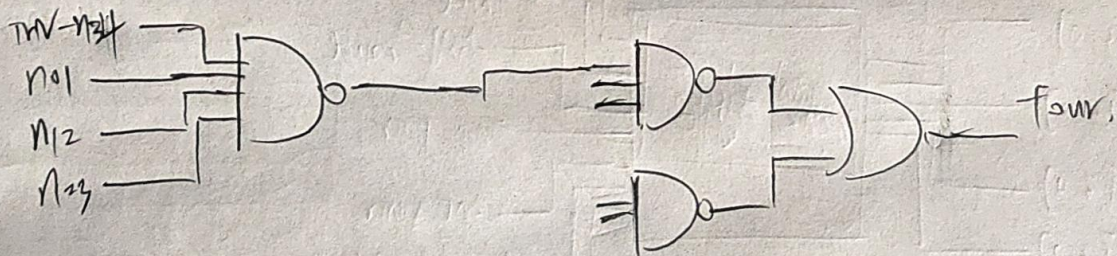


* for output "three" \Rightarrow check $C_3^5 = 10$ cases

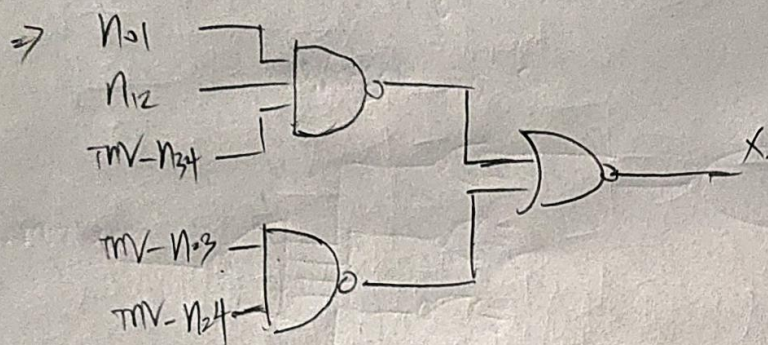\Rightarrow for example: 012/3/4 which representing $n_{01}=n_{12}=1$, $\neg n_{34}=1$,
 $\neg n_{23}=1$, $\neg n_{24}=1$



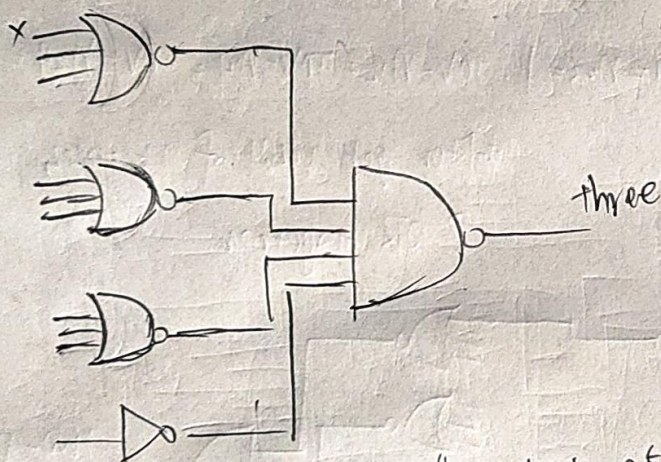
after get all result of 10 cases \Rightarrow OR together.



* for output "full-house" \Rightarrow check $C_3^5 = 10$ cases


for example: 012/34 $\Rightarrow n_{01}=n_{12}=n_{34}=1$, $\neg n_{23}=1$

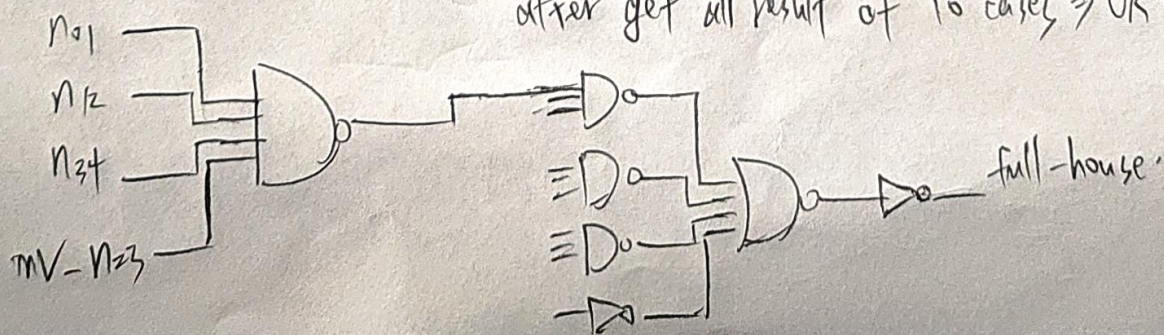after get all result of 10 cases \Rightarrow OR together




* for output "one-pair" \Rightarrow check $C_2^5 = 10$ cases.

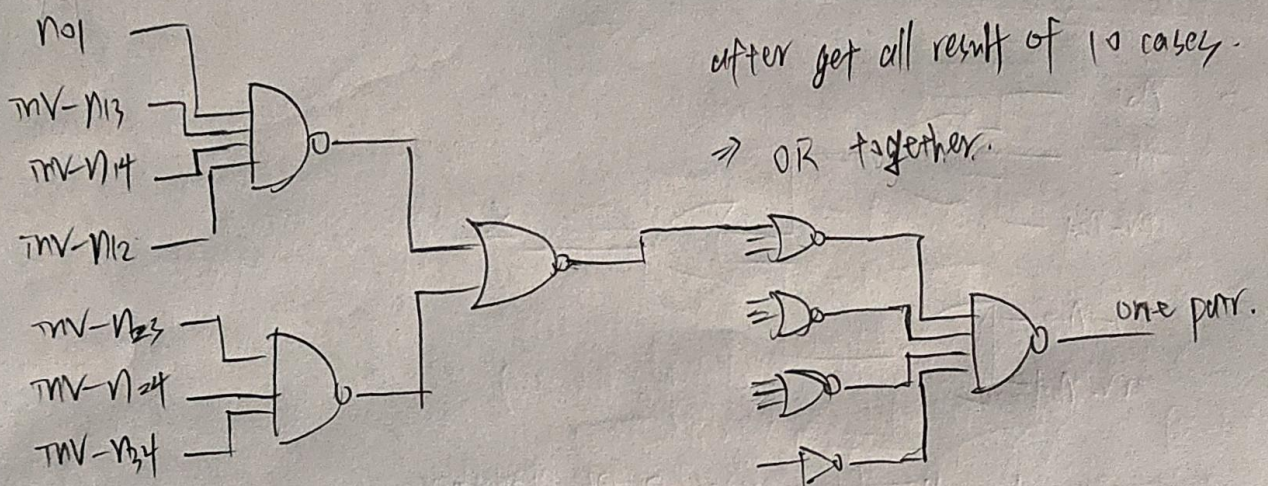for example: $01/2/3/4 \Rightarrow n_{01}=1$ $\neg n_{12} = \neg n_{13} = \neg n_{14} = 1$
 $\neg n_{23} = \neg n_{24} = \neg n_{34} = 1$




* for output "two-pair" \Rightarrow check $C_2^5 \times C_2^3 / 2 = 15$ cases.

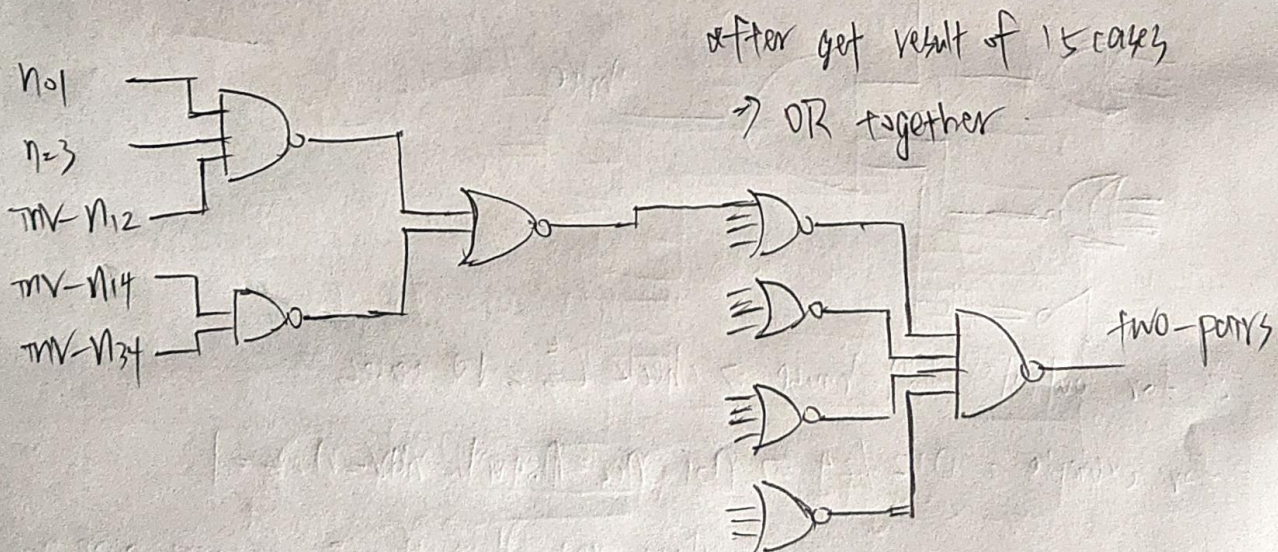for example: $01/23/4 \Rightarrow n_{01} = n_{23} = 1$ $\neg n_{12} = \neg n_{14} = \neg n_{34} = 1$



* for output "straight" $\Rightarrow 12345 \Rightarrow 10 \ 11 \ 12 \ 13 \ 1$ have 10 cases

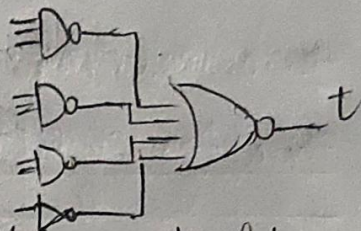
first need to check total 10 $\Rightarrow \text{inv} - \text{inv} = 1 \Rightarrow$
(because five cards have different rank).



for example $\{1 \ 2 \ 3 \ 4 \ 5\}$ - check if every cards is in the list


truth table: if $T_0 (3=0)$ is in the list $\{1-2-3-4-5\}$

	X_3	X_2	X_1	X_0	$\bar{T}_i = 1$
(0)	0	0	0	0	X
(1)	0	0	0	1	1
(2)	0	0	1	0	1
(3)	0	0	1	1	1
(4)	0	1	0	0	1
(5)	0	1	0	1	1
(6)	0	1	1	0	0
(7)	0	1	1	1	0
(8)	1	0	0	0	0
(9)	1	0	0	1	0
(10)	1	0	1	0	0
(11)	1	0	1	1	0
(12)	1	1	0	0	0
(13)	1	1	0	1	0
(14)	1	1	1	0	X
(15)	1	1	1	1	X

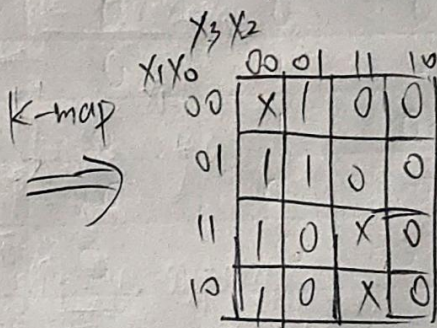


$$\Rightarrow \bar{T}_i = X_3' X_2' + X_3' X_1'$$

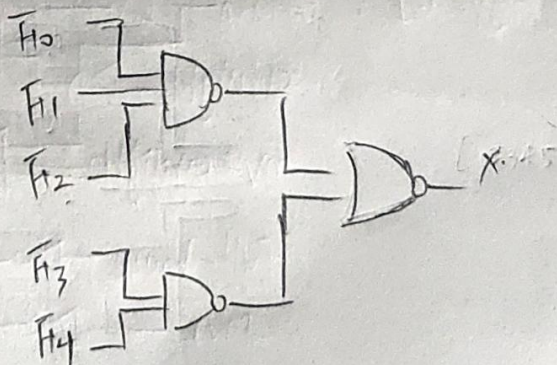for every T_0, T_1, T_2, T_3, T_4 - result



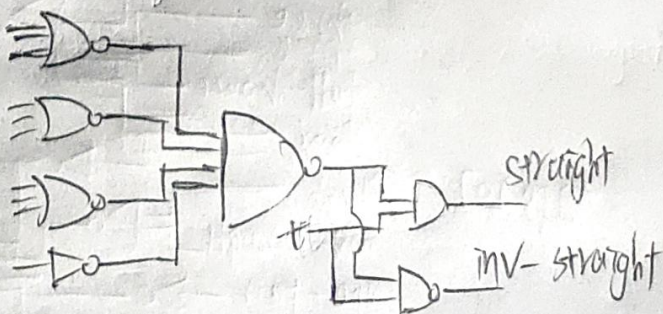after get all result of 10 cases \Rightarrow OR.



module : card type

truth table : (not complete)

flush	four	three	full-house	two-pair	one-pair	straight	type			
							[3]	[2]	[1]	[0]
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	1	0	0	0	0	1	0
0	0	1	0	0	0	0	0	0	1	1
0	0	0	0	0	0	1	0	1	0	0
1	0	0	0	0	0	0	0	1	0	1
0	0	0	1	0	0	0	0	1	1	0
0	1	0	0	0	0	0	0	1	1	1
1	0	0	0	0	0	1	1	0	0	0

⇒ type [3] : flush straight

type [2] :

type [1] :

type [0] :

Discussion: how to improve critical path

1. 盡量把 AND 和 OR gate 轉換成 NAND 和 NOR gate。
2. 因為 delay 取決於路徑上 gate 數量，盡量不要疊太多的 gate。
3. 把所有可能的 case 都攤開來平行的做，可以減少 delay。
4. 如果 AND 或 OR 的 input 太多的話，拆成多級，每個 gate input 平均且少

Ex OR 15 \rightarrow NOR4 * 3 + NOR3 + NAND4

OR 10 \rightarrow NOR3 * 3 + NAND4