




4. (20%) For the following transmission-gate circuit,

(a) (10%) Please show the function of this circuit.

*Hint: You can use the truth table method to find the function of Y.*


(b) (10%) Is there any bad-zero or bad-one problem in this circuit? **Explain why.** (Bad-one means the voltage of logic-1 is only  $V_{DD} - V_{tn}$ ; bad-zero means the voltage of logic-0 is  $|V_{tp}|$  )

 

 5. (10%) For the following I-V curves of an NMOS transistor, given the slope at

0 for the top three curves, estimate a precise value of  $V_t$  (小數點以下兩位).

Explain how you find this value from the three slopes.



6. (15%) A 3-input minority gate returns output “1” if no more than two of the inputs are “1”.

(a) (5%) Sketch a **transistor-level** circuit diagram for a 3-input minority gate using a single stage of CMOS static logic. Please use the least number of

transistors. Note that all three inputs and their complements are available for this circuit.

- (b) (10%) Design a 3-input minority gate using CMOS **NANDs**, **NORs**, and **inverters**. Compare the numbers of transistors required in (a) and (b).

TA：陳丕全，EE2-329

TA email: r11943013@ntu.edu.tw

HW1 Office hours: 10/3 14:00-16:00 @電二 329 室

10/4 14:00-16:00 @電二 329 室

If you have no time during office hours, you can email TA to discuss another time for an appointment.